



虎尾科技大學

Date : 2011/11/29

O2Micro- Intelligent Lighting


# Subject---Innovation /Creation

- Think Different

- Make Different




# Steve Jobs

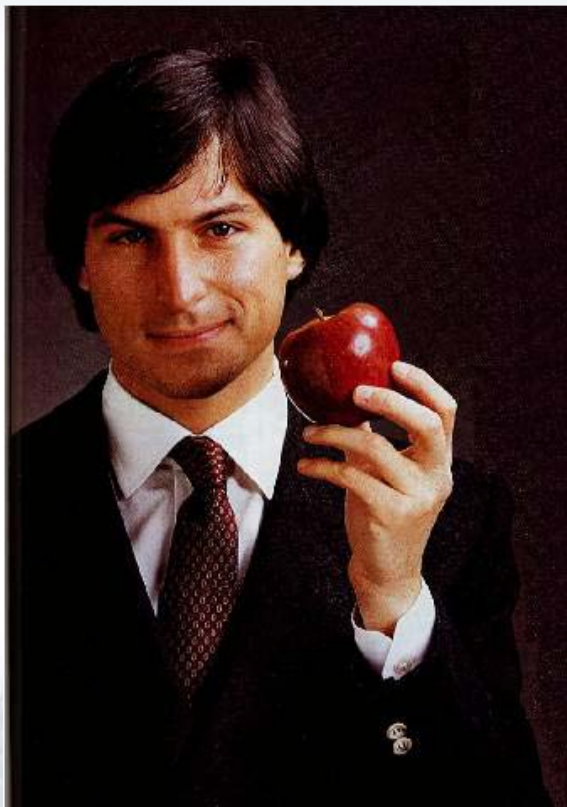

# In Apple – MacBook Air

## 创新薄

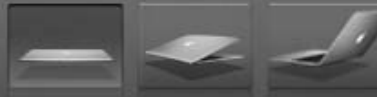

全新的 MacBook Air  
更佳图形性能，更大存储空间，仍是全球超薄的笔记本电脑。

全新的 MacBook Air 现配备了更大的硬盘、较之前提升四倍的图形性能、以及更强劲动力，为你的日常工作生活提供源源动力，却依然轻薄极致，超乎想象。超大的空间得以容纳更多可能。MacBook Air 再度改写移动计算的标准。



[观看演示之旅 ▶](#)



# In Apple---I Pad, I Mac



# Three Cases of My Experience---Case I




# ***Inverter structure and principle***



# Two stages Buck/Royer Oscillator Inverter(1954)

Self Oscillator

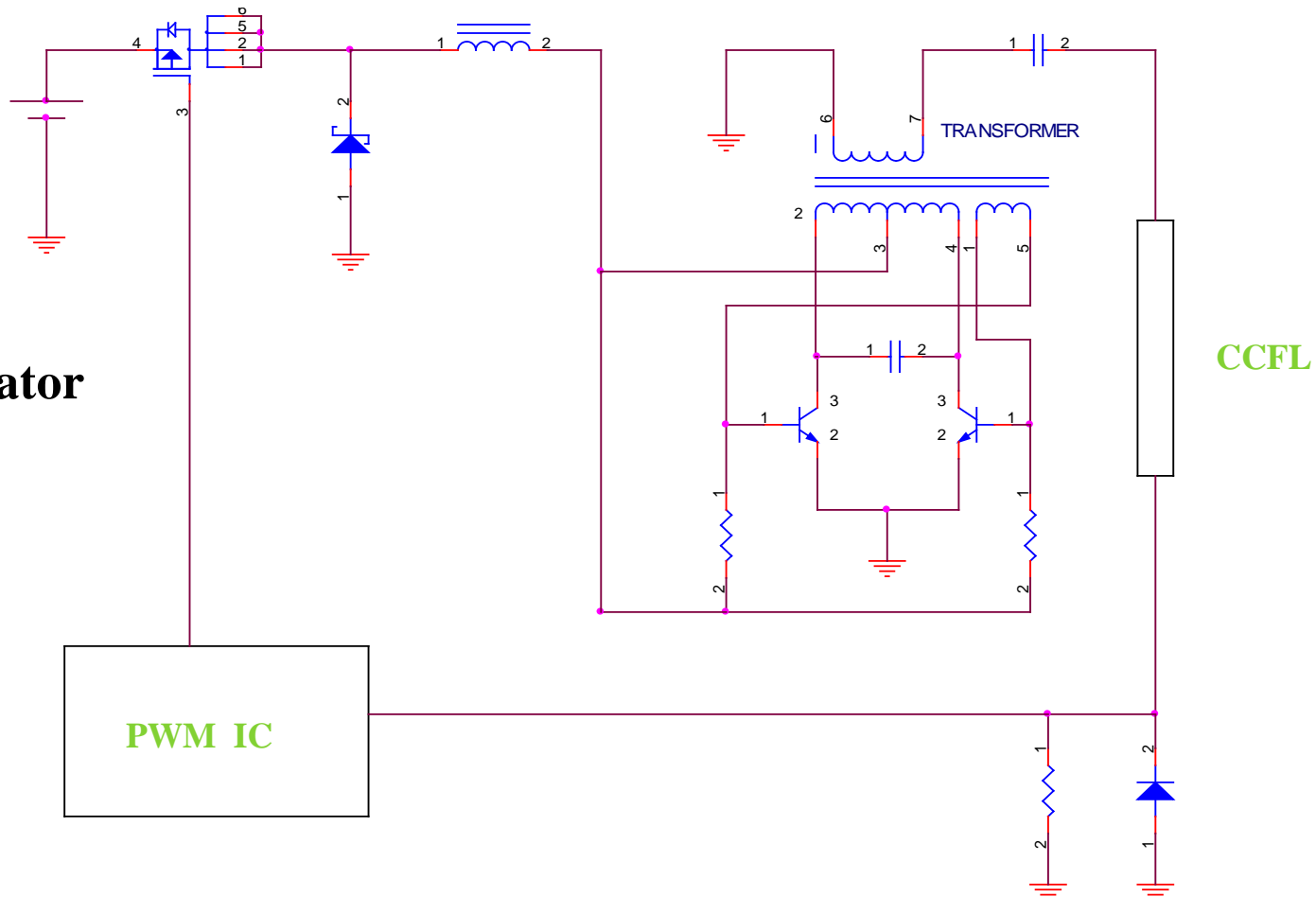




## Royer Weakness:


- 1. Low efficiency**
- 2. High temperature**
- 3. Complex transformer**
- 4. High voltage operation**
- 5. Vary operating frequency**

# Single Stage Full Bridge Inverter

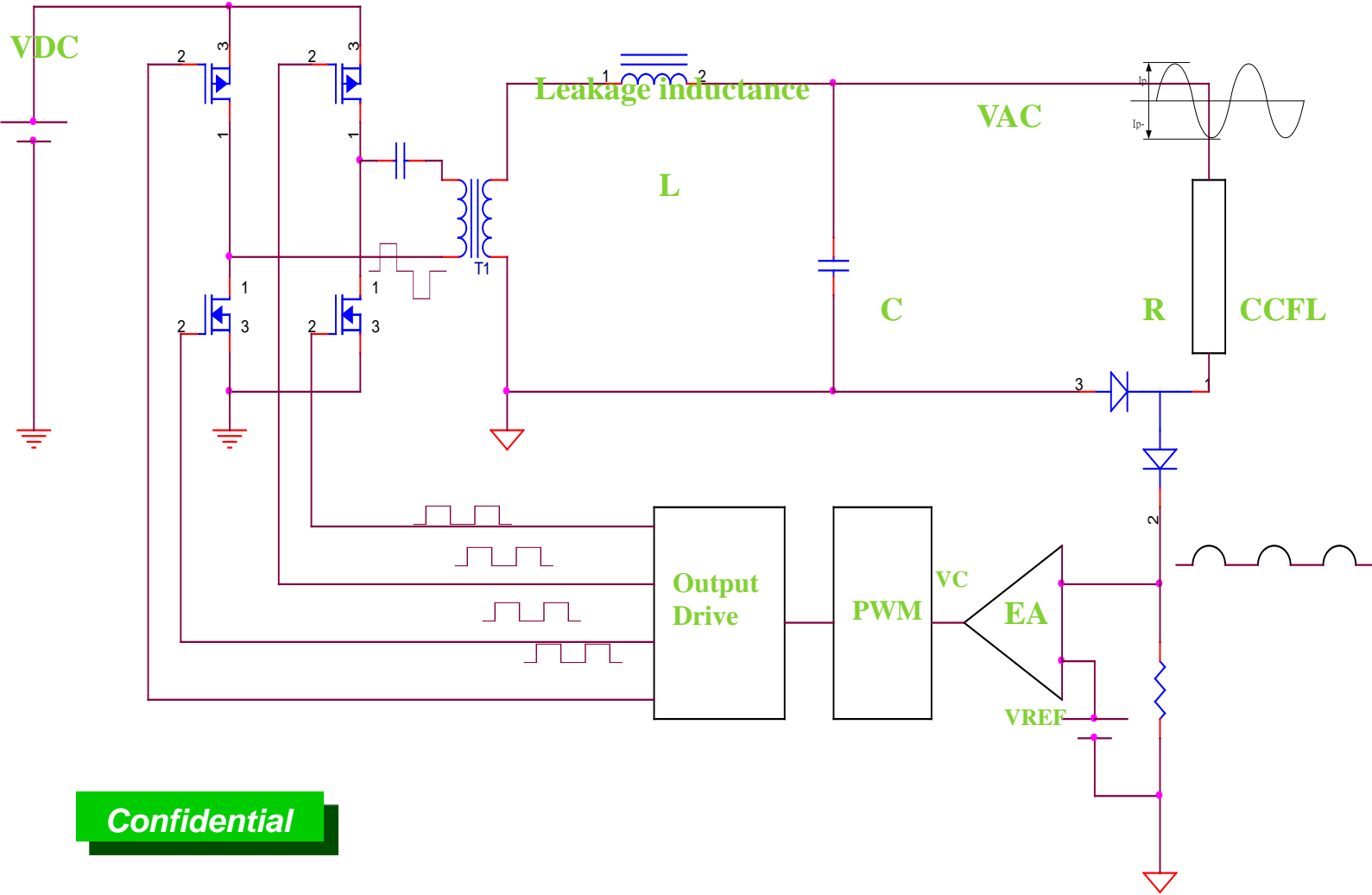

**Confidential**

# Inverter structure

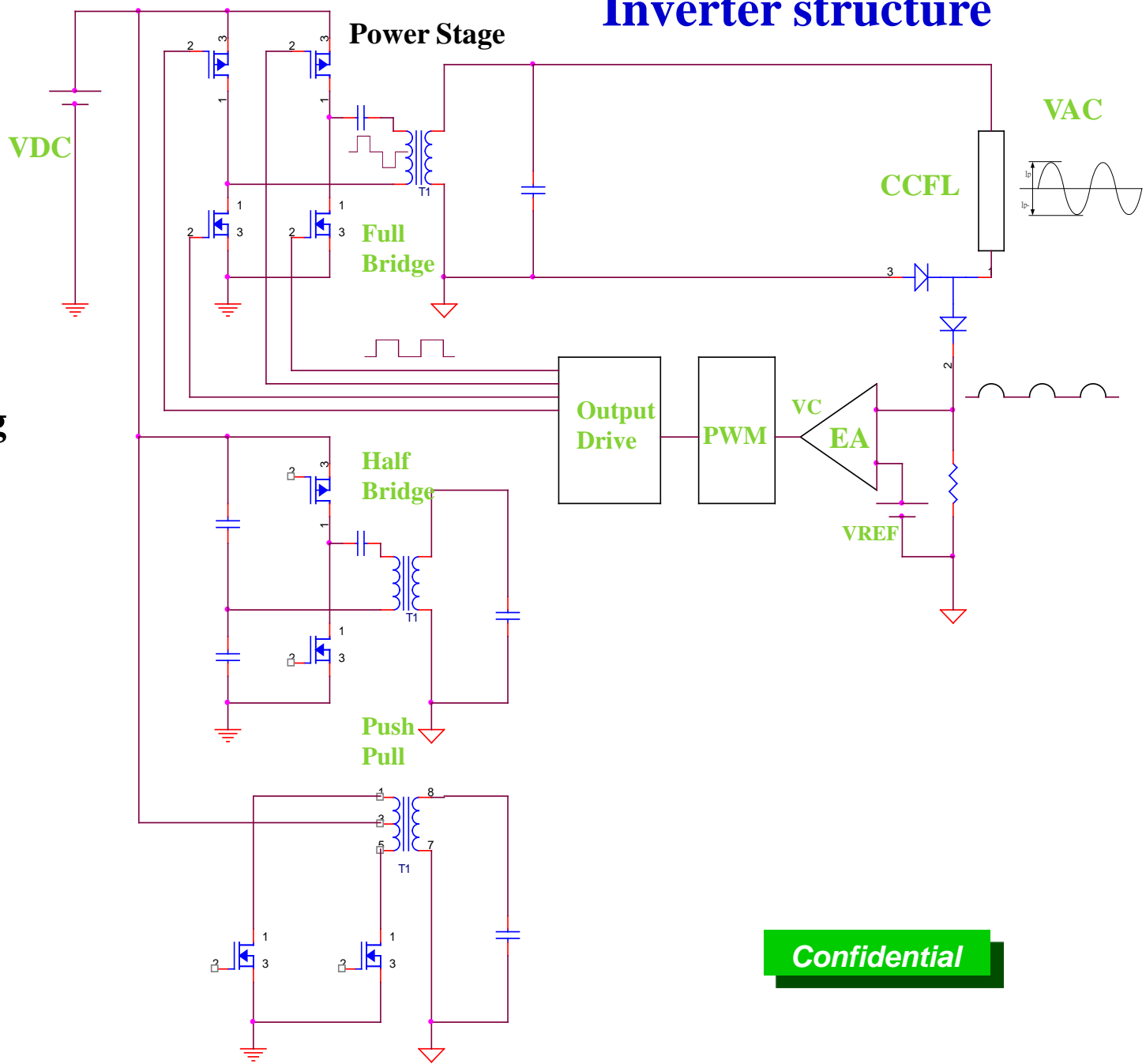


Extra Driving

**Confidential**

## Features:

1. High efficiency.
2. Simple transformer.
3. Low temperature.
4. High reliability.
5. Small board side
6. Low operating voltage.

## Phase-Shift Full-Bridge Inverter

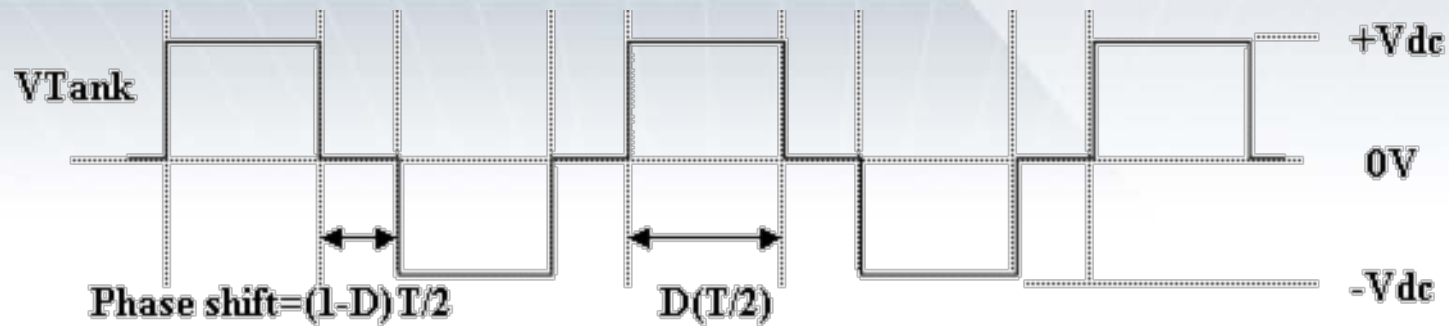

- The fundamental component of the voltage applied to the tank:

$$V_1 = \frac{4}{\pi} \cdot V_{in} \cdot \sin\left(\frac{\pi}{2} \cdot D\right) \cdot \sin(\omega_{sw} \cdot t)$$


- The output voltage of the inverter :

$$V_{out(rms)} = N \cdot M(\omega_n, Q) \cdot \frac{2\sqrt{2}}{\pi} \cdot V_{in} \cdot \sin\left(\frac{\pi}{2} \cdot D\right)$$

$M(\omega_n, Q)$  is the inverter voltage gain;  $N$  is the turn ratio of the transformer.



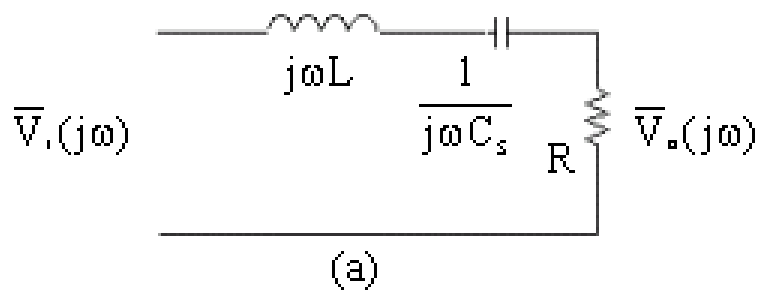
# Background- Resonant Inverter for CCFLs




$$\left| \frac{\bar{V}_o(j\omega)}{\bar{V}_i(j\omega)} \right| = \frac{1}{\sqrt{1 + Q_s^2 \left( \frac{\omega}{\omega_s} - \frac{\omega_s}{\omega} \right)^2}}$$
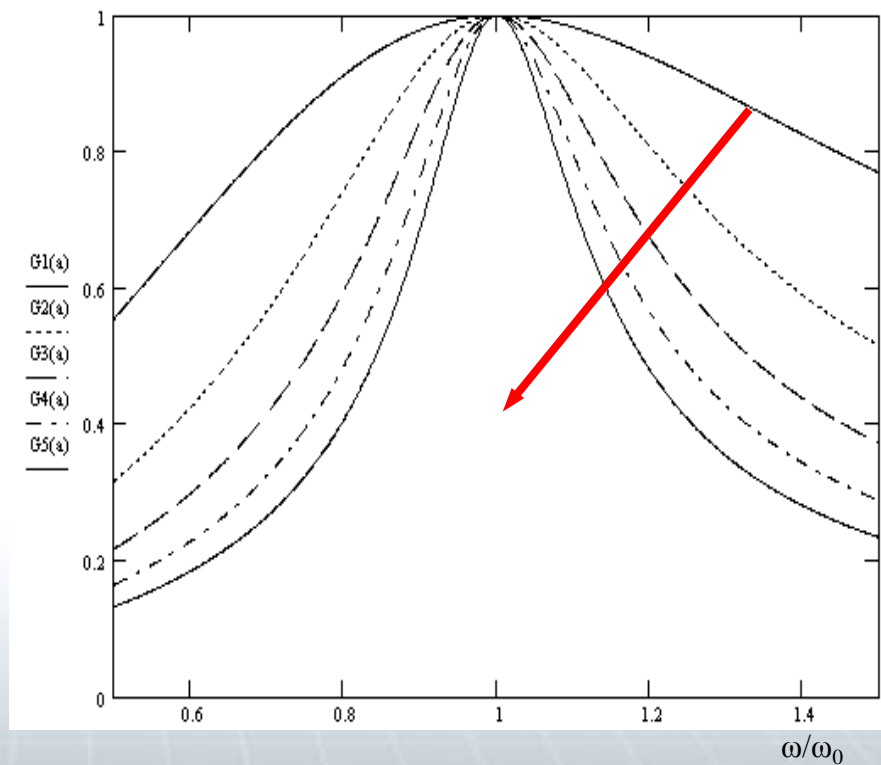
$$\omega_s = 1/\sqrt{LC_s} \quad Q_s = \omega_s L/R = 1/\omega_s C_s R$$




## SLR Circuit Topology
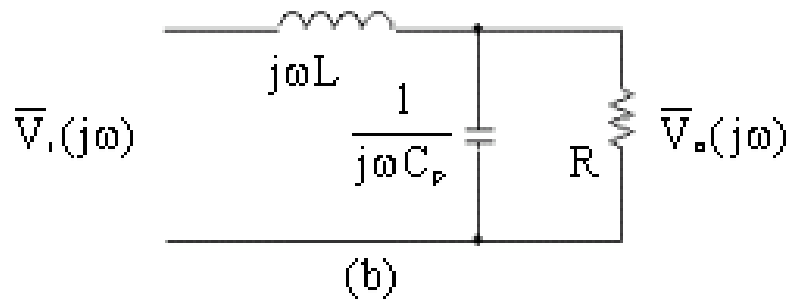
# Background- Resonant Inverter for CCFLs




$$\left| \frac{\bar{V}_o(j\omega)}{\bar{V}_i(j\omega)} \right| = \frac{1}{\sqrt{\left(1 - \left(\frac{\omega}{\omega_p}\right)^2\right)^2 + \left(\frac{\omega}{\omega_p Q_p}\right)^2}}$$
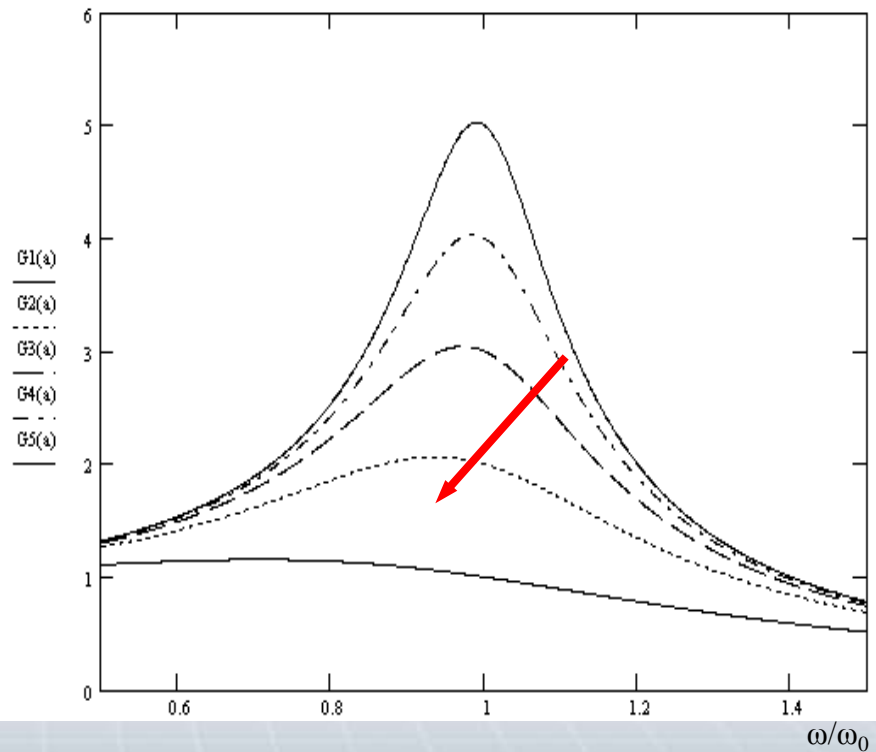
$$\omega_p = 1/\sqrt{LC_p} \quad Q_p = R/\omega_p L = \omega_p C_p R$$




## PLR Circuit Topology
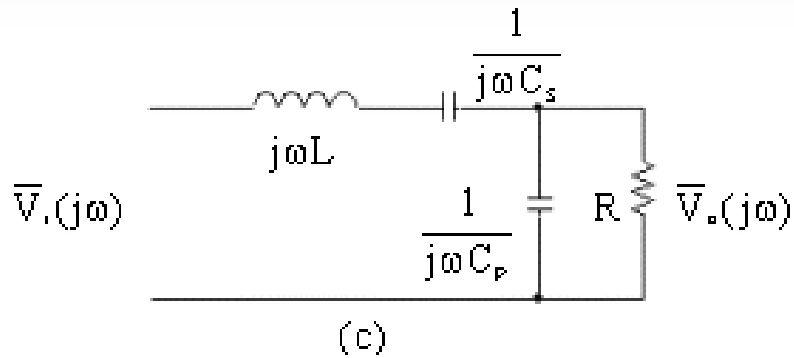
# Background- Resonant Inverter for CCFLs





$$\frac{|\bar{V}_o(j\omega)|}{|\bar{V}_i(j\omega)|} = \frac{1}{\sqrt{\left(1 + \frac{C_p}{C_s} - \left(\frac{\omega}{\omega_p}\right)^2\right)^2 + Q_s^2 \left(\frac{\omega}{\omega_s} - \frac{\omega_s}{\omega}\right)^2}}$$

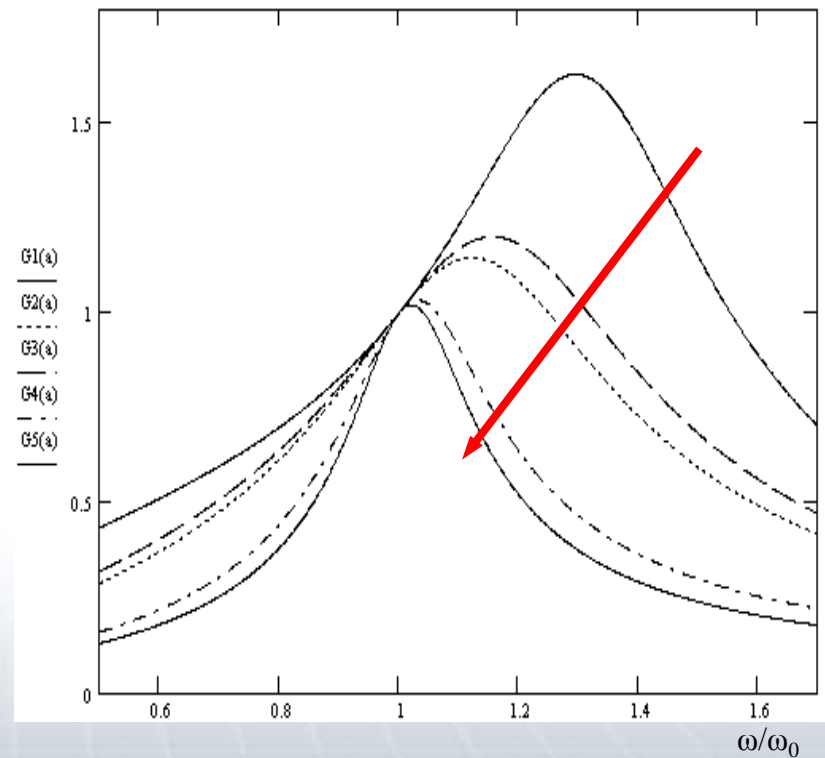


## SPLR Circuit Topology
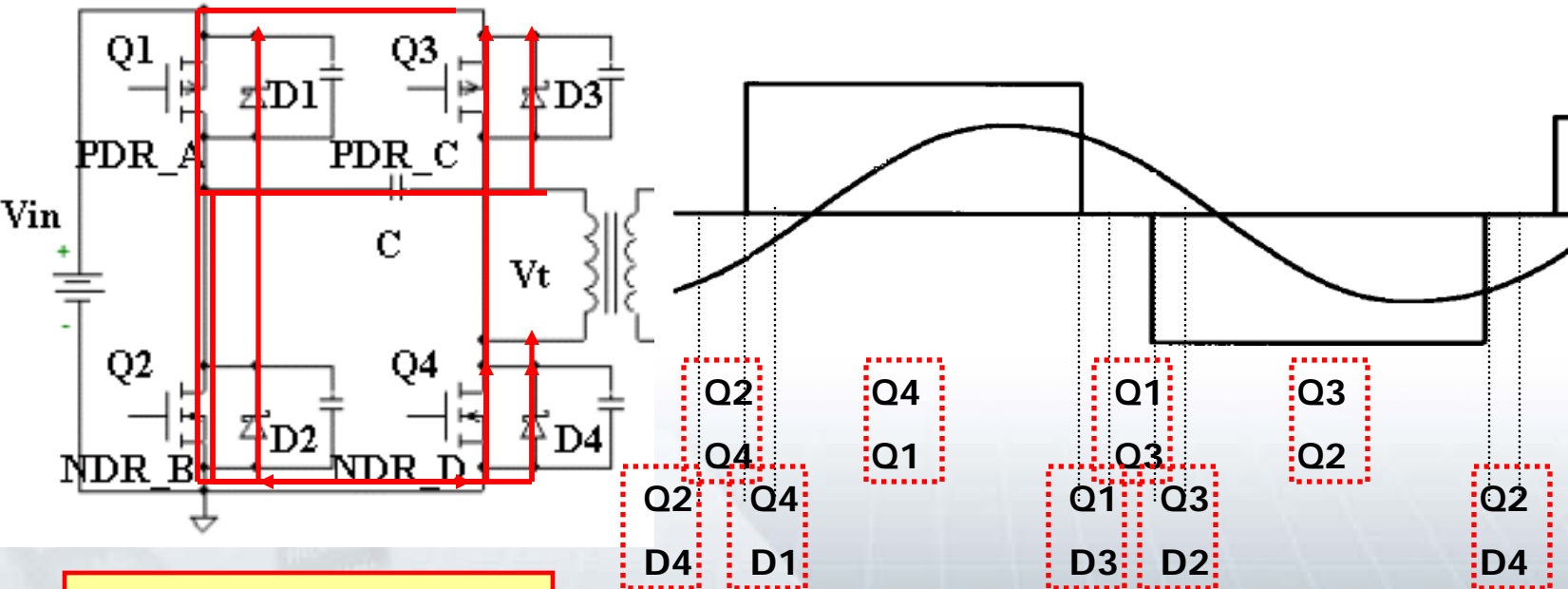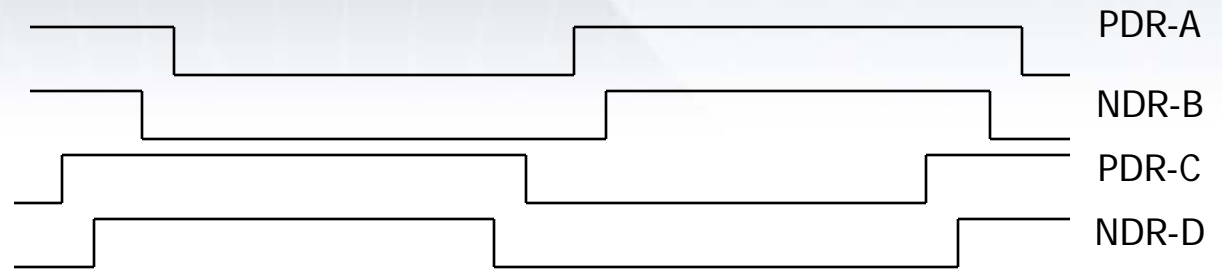
# Phase-Shift Full-Bridge Inverter- Add Dead Time



**4 ZVS on**

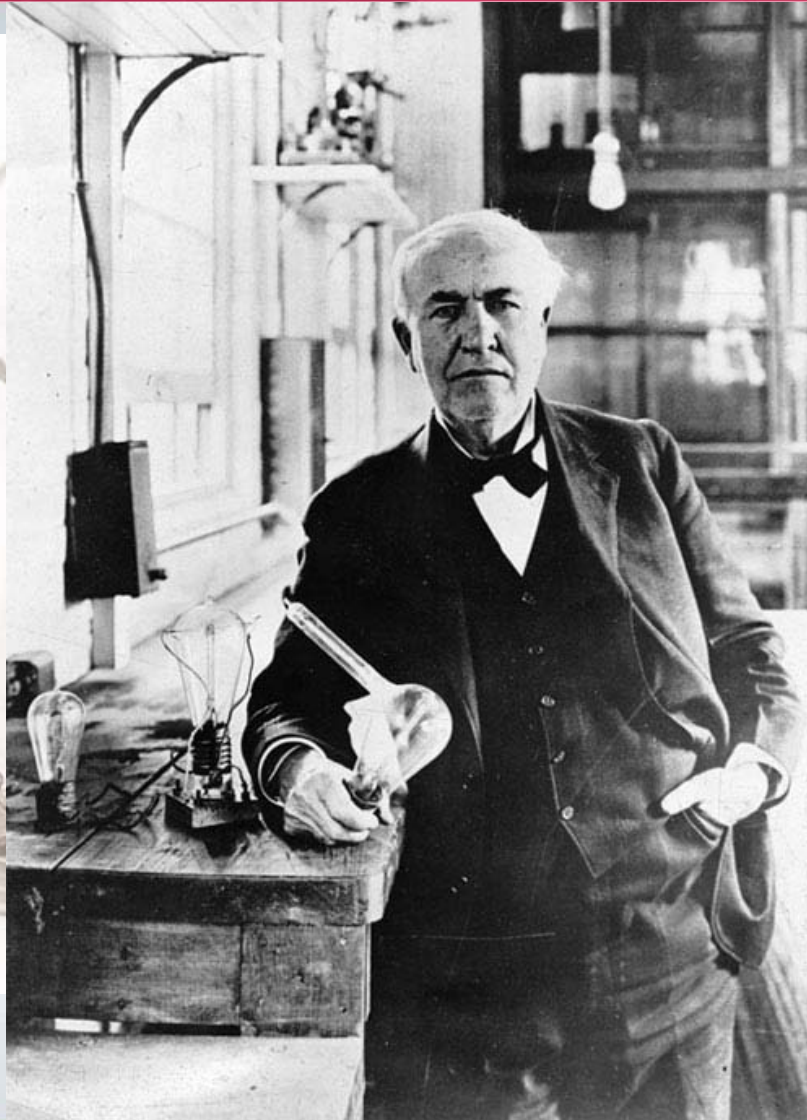

美國專利第223898號，電燈





# LED三段调光技术

第一阶：100%亮度

第二阶：50%亮度

第三阶：25%亮度

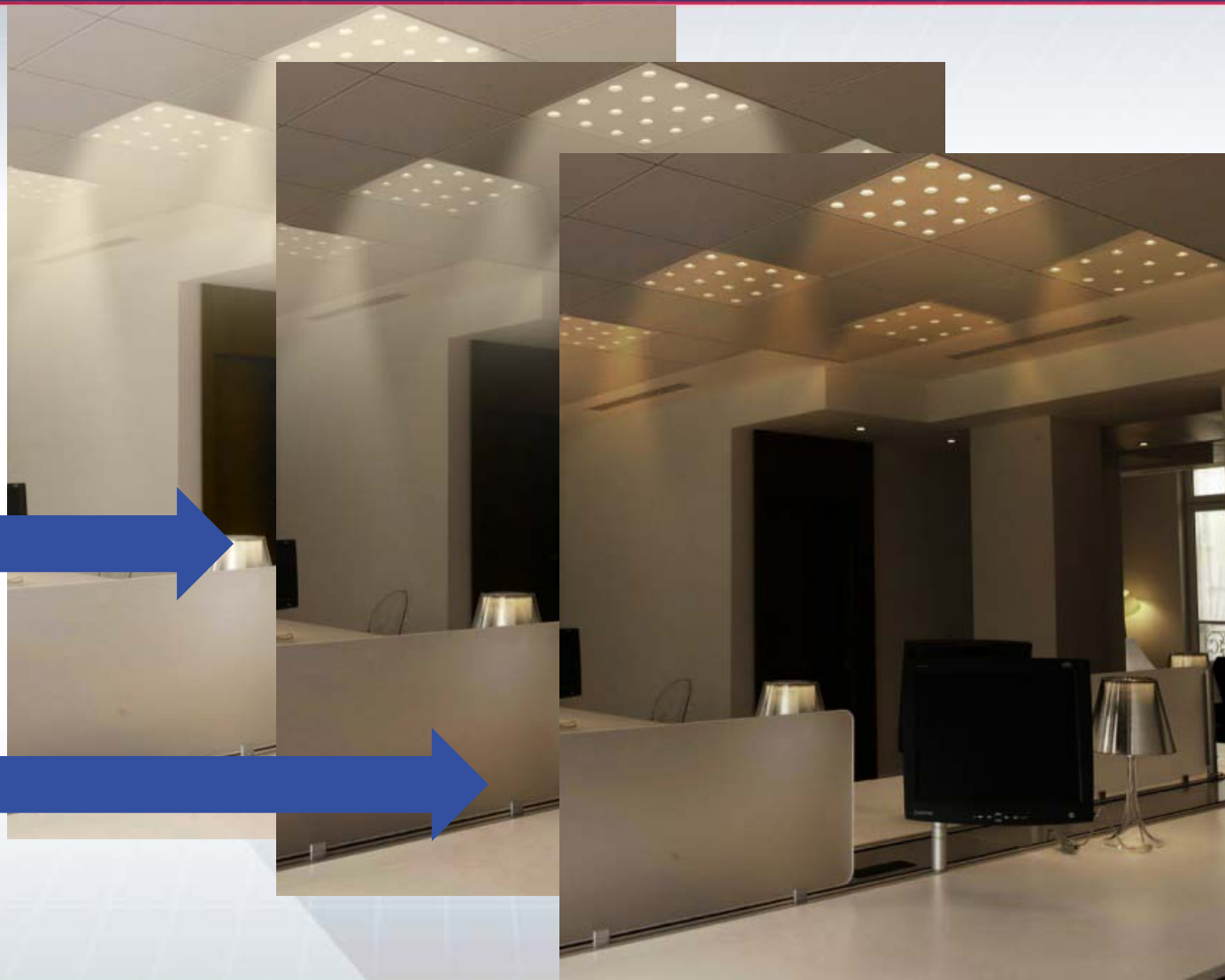

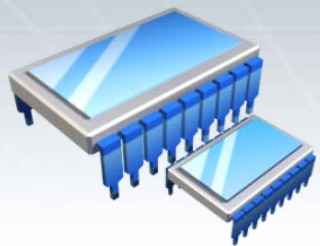


# 需要额外的元器件吗？



**不需要!**

# 常见的光照情况

不是所有时间, 我们都需要全亮度的照明

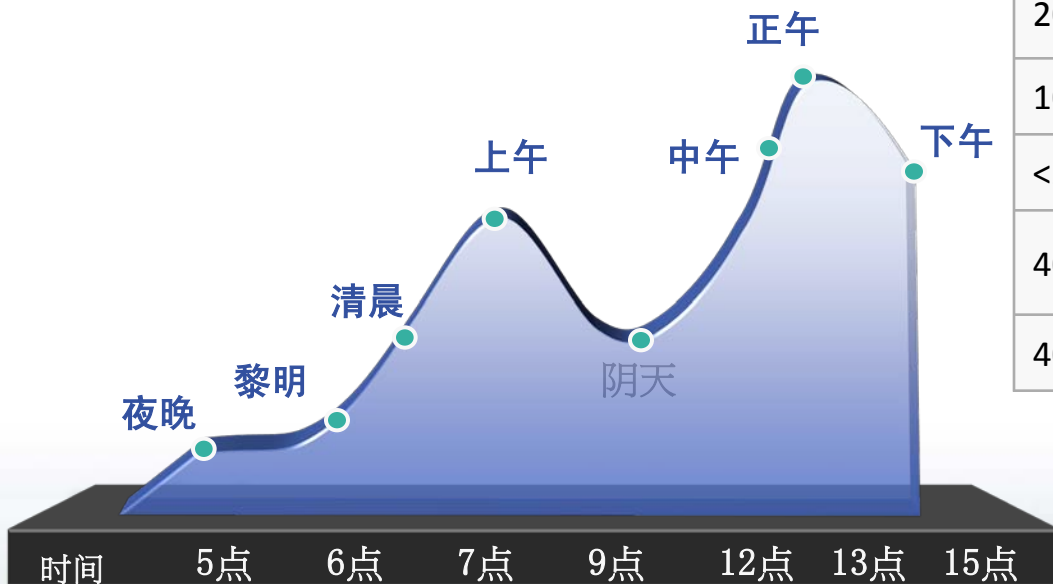

室外照度	例子
120,000勒克斯	最亮的阳光
110,000勒克斯	明亮的阳光
20000勒克斯	湛蓝的天空, 正午
10,000 - 15,000勒克斯	阴天, 中午
<200勒克斯	黑暗的风暴雨, 中午
400勒克斯	晴天, 日出或日落
40勒克斯	全阴, 日出或日落

# 一个普通人的照明需求分析

一个人全天（每天约16小时）照明需求分析：

1

上午时段 07:00-12:00  
下午时段 14:00-17:00  
此时段所需照明强度

**50%**

使用O2第二段照明模式  
与传统LED相比,节省

**1/2**

2

中午时段 12:00-14:00  
此时段所需照明强度

**25%**

使用O2第三段照明模式  
与传统LED相比,节省

**3/4**

3

晚餐后时段17:00-23:00  
此时段所需照明强度

**100%**

使用O2第一段照明模式  
与传统LED相比,节省

**0**

# 为每人每天节能

使用三阶调光技术的LED灯

相当于只需3W的LED照明

就能满足单人全天的照明需求





# 为家庭减轻负担

假设一个家庭，三房两厅两卫，共使用80W LED灯具  
平均照明使用16小时，家庭电费0.65元/度

使用传统LED  
一天耗电1.25度  
每天电费0.82  
全年照明费用约  
300元

**Vs**

使用O2三段LED  
一天耗电0.625度  
每天电费0.41  
全年照明费用约  
150元

每年能为每户家庭节省

**150元**



# 为国家节约能源

使用三阶调光技术的LED灯

中国全年约省电：**470亿千瓦时**

相当于三峡水电站半年发电量

全年节煤：**1700万吨**



# 已投入市场的产品

## OZ9995 Inside

**長寿命 & 省エネ**  
 一灯の電球と比較して約40倍の長寿命。  
 消費電力は約1/8。  
 長時間使用が疲れにくい新に  
 対応します。

**環境にやさしい**  
 水銀ゼロCO<sub>2</sub>削減  
 一年中電球を60W相当の明るさLED電球  
 10W電球に変換するだけで、家庭全体の  
 電球が10W一般電球600Eに相当する  
 CO<sub>2</sub>削減につながります。

**安心安全**  
 電球が一つ落ちて  
 いる場合でも、  
 ほかの電球が  
 落ちる心配が  
 ありません。

**すぐに明るく**  
 1秒で明るい状態が  
 実現します。しかも  
 カンパイルタイプ  
 の電球は、  
 電球が  
 落ちる心配が  
 ありません。

**低  
 発熱**  
 発熱が少なく、  
 周囲の温度が  
 上昇しにくく、  
 安心して  
 使用できます。

**電球代  
 比較**

**明るさ3段階切替  
 昼白色使用の場合**

明るさ	消費電力	寿命	電球代
100%	6.8W	約2,312年	約2,312円/年
50%	3.5W	約674年	約1,310円/年
20%	1.5W	約289年	約674円/年

※電球代は1灯あたりを基準として算出しています。電球の価格や寿命はメーカーによって異なります。

**電球安全上の注意 屋内専用**

**注意**

- 電球の破損、落下、破裂による怪我や火災の原因となります。破損防止のため、電球の取付けには必ず取扱説明書に従って正しく取付けます。
- 電球の取付けには必ず取扱説明書に従って正しく取付けます。
- 電球の取付けには必ず取扱説明書に従って正しく取付けます。

**ご使用上の注意**

- 電球の取付けには必ず取扱説明書に従って正しく取付けます。
- 電球の取付けには必ず取扱説明書に従って正しく取付けます。
- 電球の取付けには必ず取扱説明書に従って正しく取付けます。

**ご購入の前に**

以下の器具には絶対に使用しないでください。

- 電球の取付けには必ず取扱説明書に従って正しく取付けます。
- 電球の取付けには必ず取扱説明書に従って正しく取付けます。
- 電球の取付けには必ず取扱説明書に従って正しく取付けます。

**オリエント電機 株式会社**  
 〒140-0525 東京都目黒区大川1丁目16番10号  
**0120-104-481**

**ORION**

照明の未来を明るく照らす。  
 ルミナスの  
**LED電球**



**ハロー! 環境技術**  
 HELLOWORLD ENVIRONMENTAL TECHNOLOGY

LED-2010-9

## OZ9992 Inside









# 小夜灯功能的LED灯泡



# LED Lighting---Free Dimming

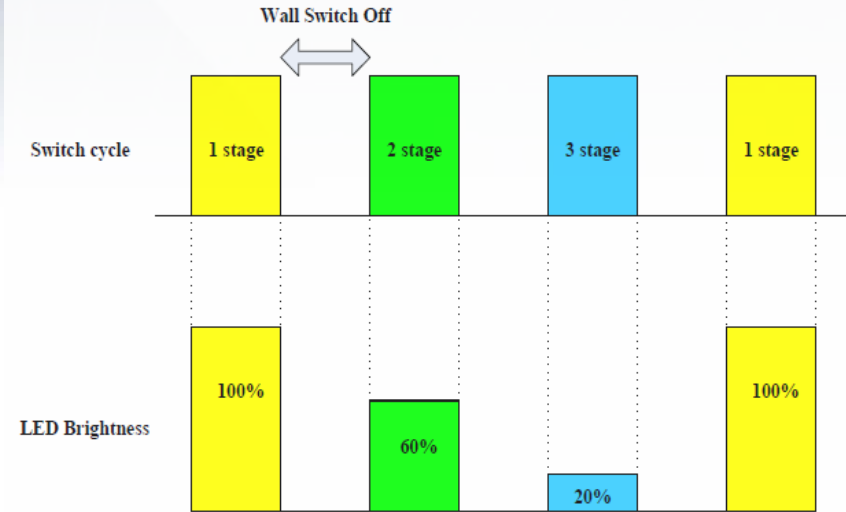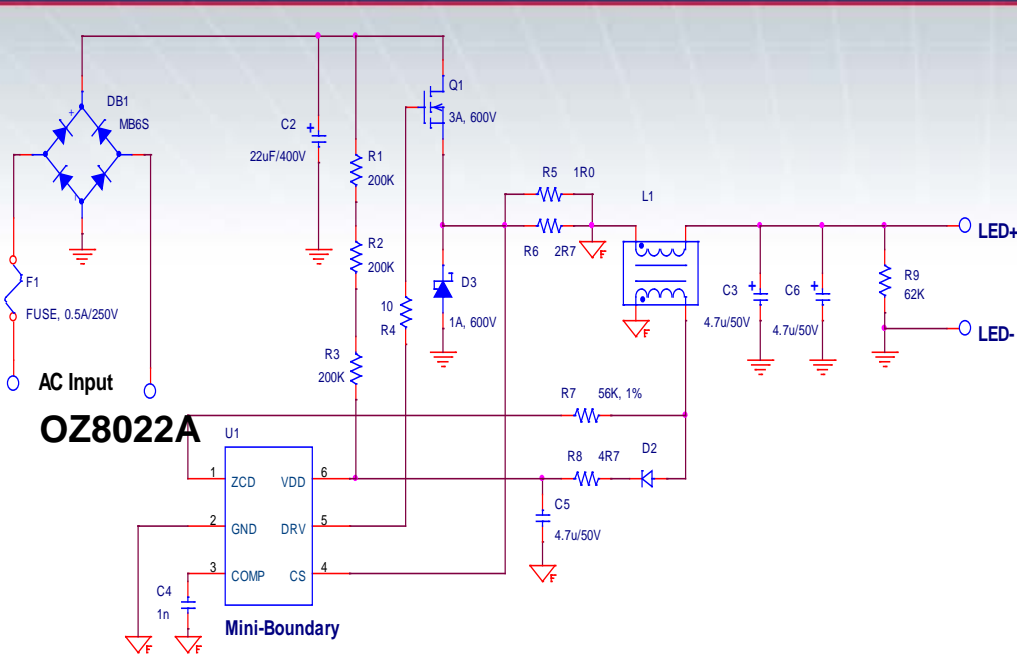

## Advantages:

- Simple, only AC wall switch
- Inexpensive, less than 20 components
- Small, can be put in E17 bulb
- Efficient, energy saving
- Compatible, free-dimming control
- NO flickering



# Case III






# Bike Lamp Solutions




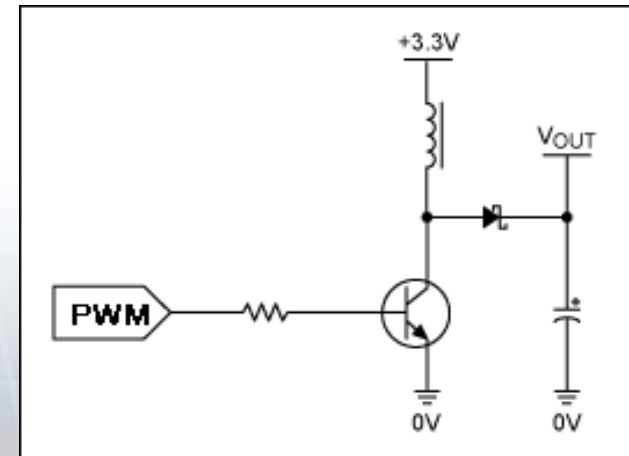
# Prior Art

- More popular within Even Alkaline pack (2 or 4)
  - Battery pack in Europe
    - Usually 2 or 4 pack on sell
  - 2 Alkaline needs boost topology
    - Popular solution
      - MCU send constant PWM control
  - More application in 1 Alkaline ( $V_{BAT} = 0.8 \sim 1.5V$ )
    - Boost voltage from 0.8V
    - Schottky diode forward voltage is above 0.6V
      - ◆ Startup voltage must above 1V



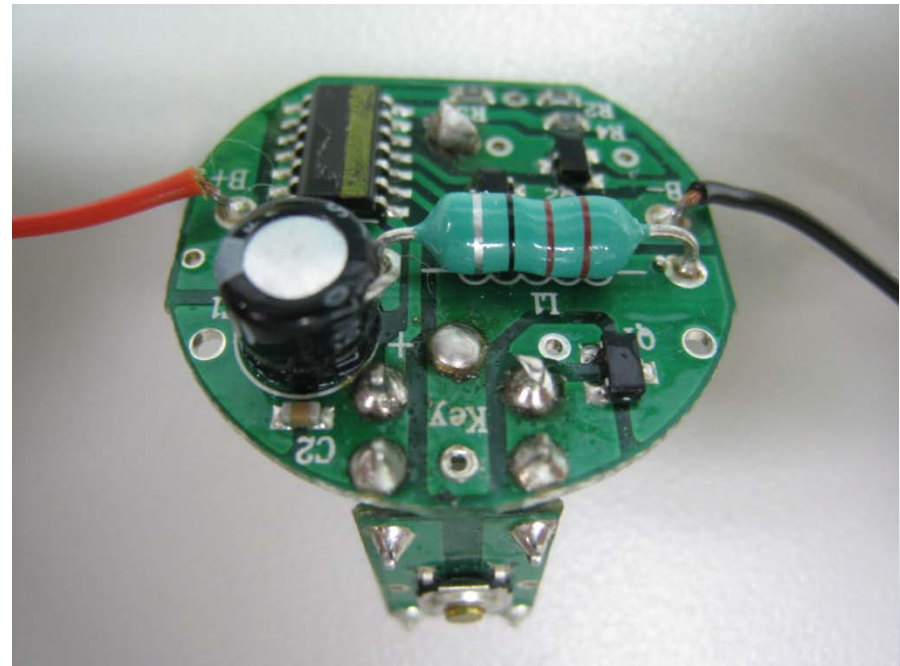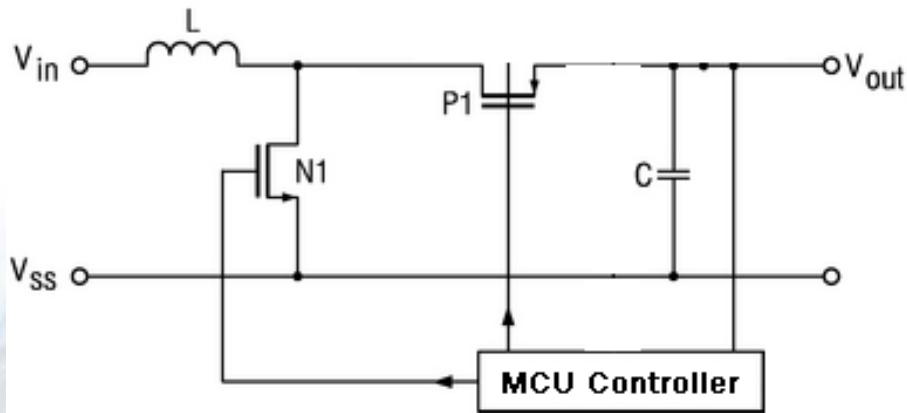
# Boost topology

- Replace Schottky diode with PMOS
  - Startup from 0.8V
- BOM list (total 11 items)
  - MCU
  - 2 MOSFET
  - Inductor



# Traditional Circuit


## Experiment Result

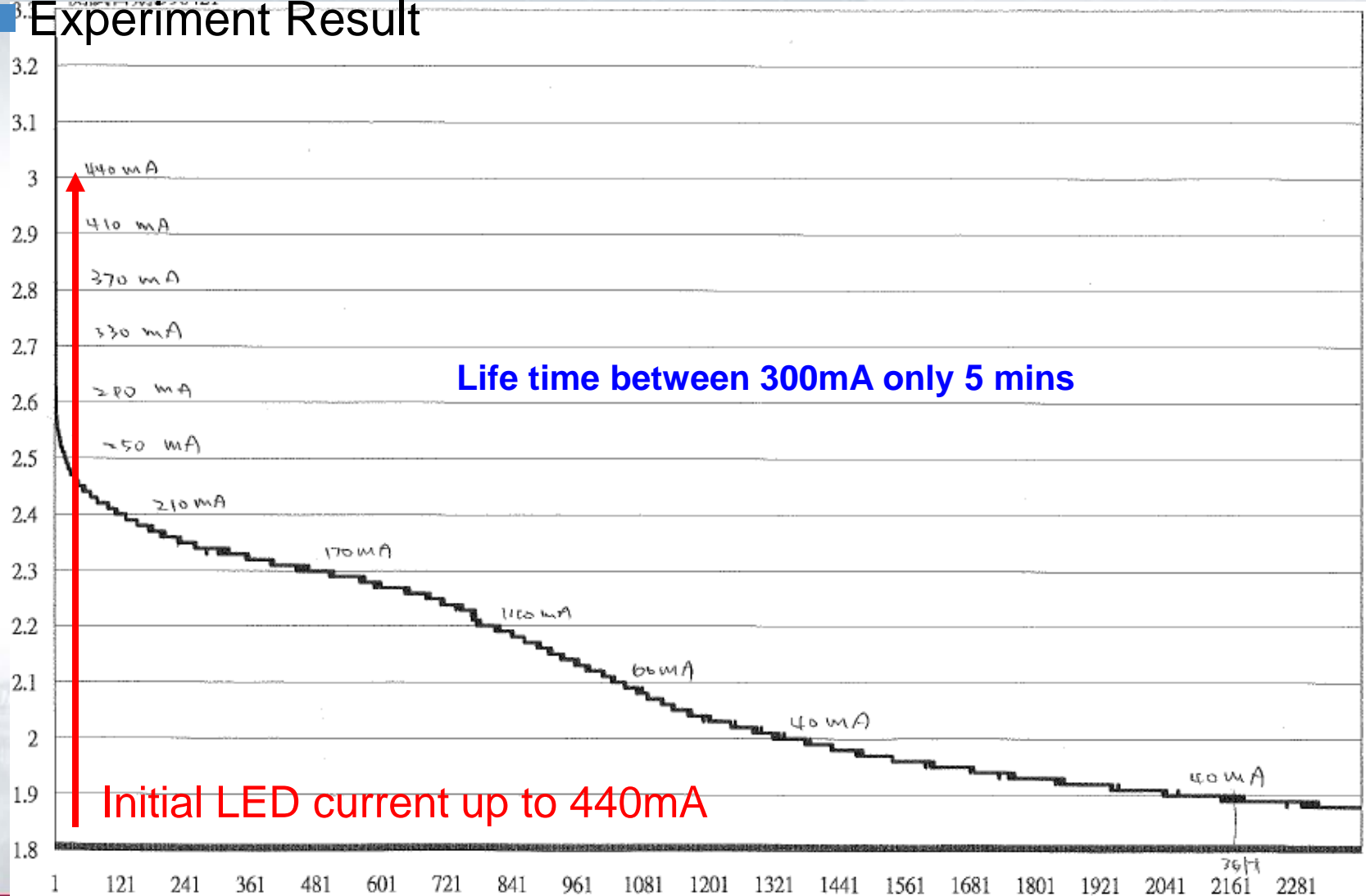

# Our Solution\_711-26
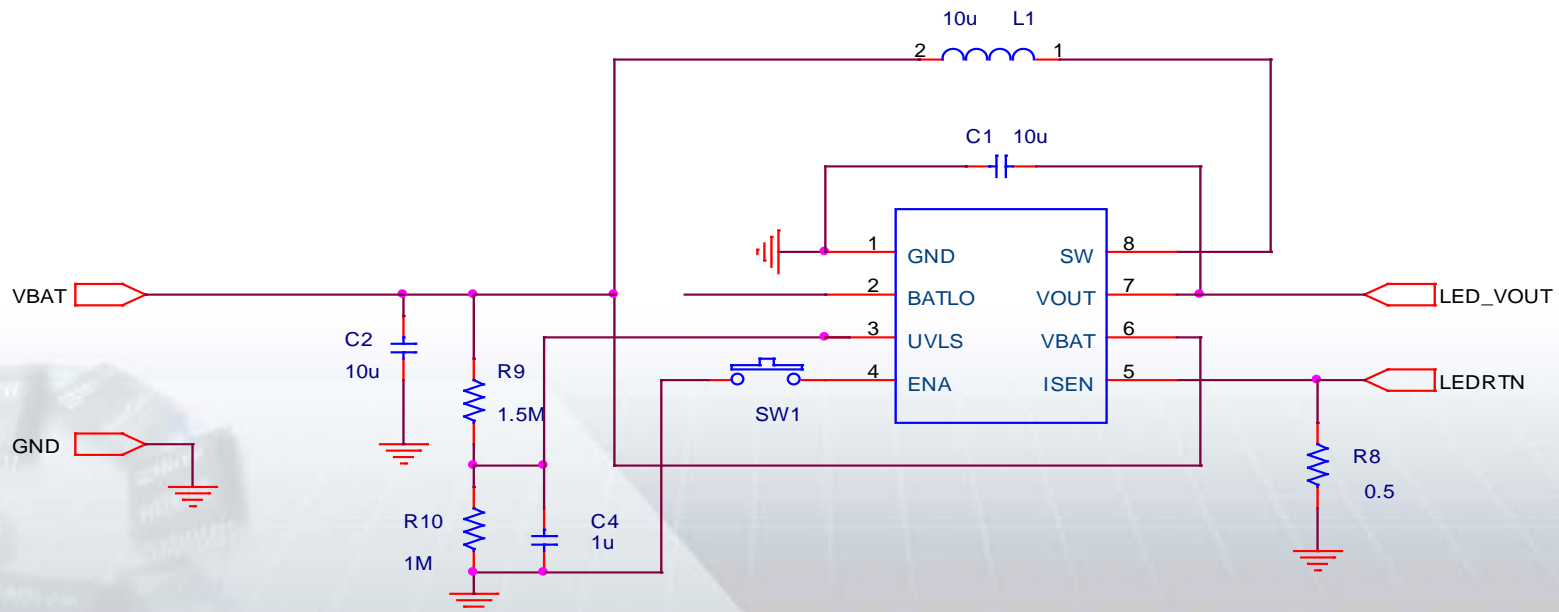
## ■ Features

- Ultra low VIN start up and operation voltage from 0.8V
  - Support one or two cell NiMH or Alkaline battery
- Minimum external component count
  - 7 items without 2 MOSFET
- Constant LED current When VBAT=0.8~3V



# Our Solution\_711-26

## ■ High Efficiency:

Vbat(V)	Iin(mA)	LED Voltage(V)	LED Current(mA)	Eff(%)
3	359	3.026	306	85.98
2.8	385	3.023	306.5	86.11
2.6	326	2.983	246.7	88.82
2.4	227	2.92	167	89.51
2.2	120	2.832	84	90.11


## ■ Current Mode:

Vin(V)	Iin(mA)	VLED(V)	ILED(mA)	Eff(%)
3	586	2.663	518	78.46
2.8	363	2.591	323	82.34
2.6	180	2.497	164	87.50



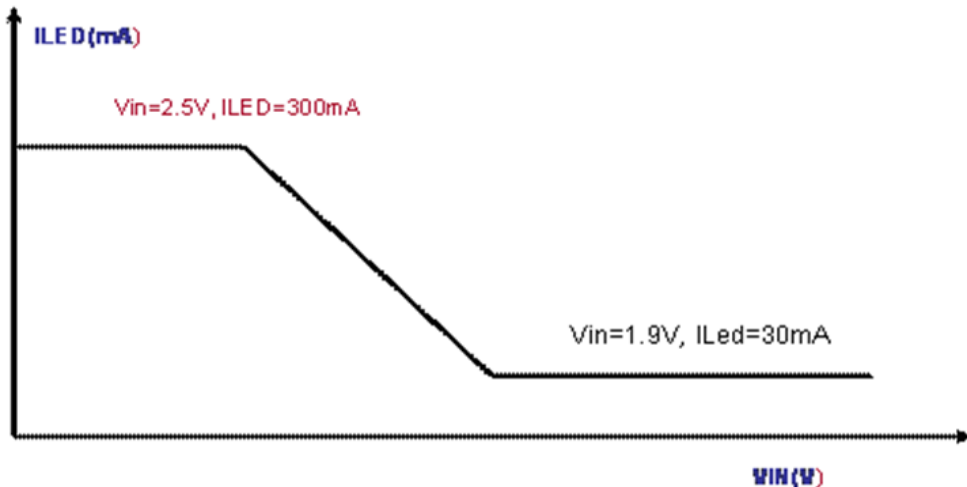
# Our Solution\_711-26

- User-defined where LED current starts to decrease
  - Extend life time
- Build in Toggle Switch Modes



Our Solution right now!

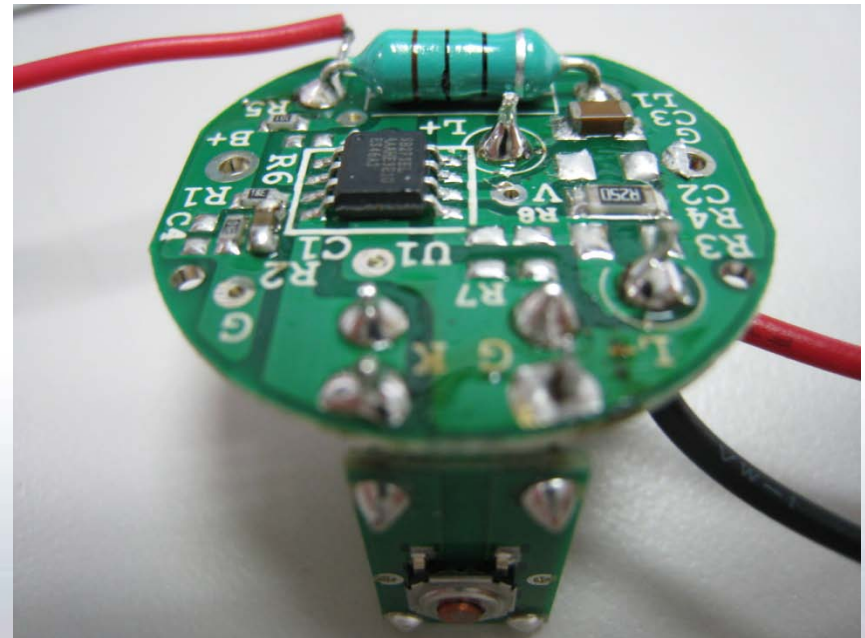

# Our Solution\_711-26


## ■ Protections

- Output Over-Voltage Protection (OVP)
- Output Short-circuit Protection (SCP)
- Over-Current Protection (OCP)
- Over-Temperature Protection (OTP)



# Our Solution\_711-26

## ■ Experiment Result

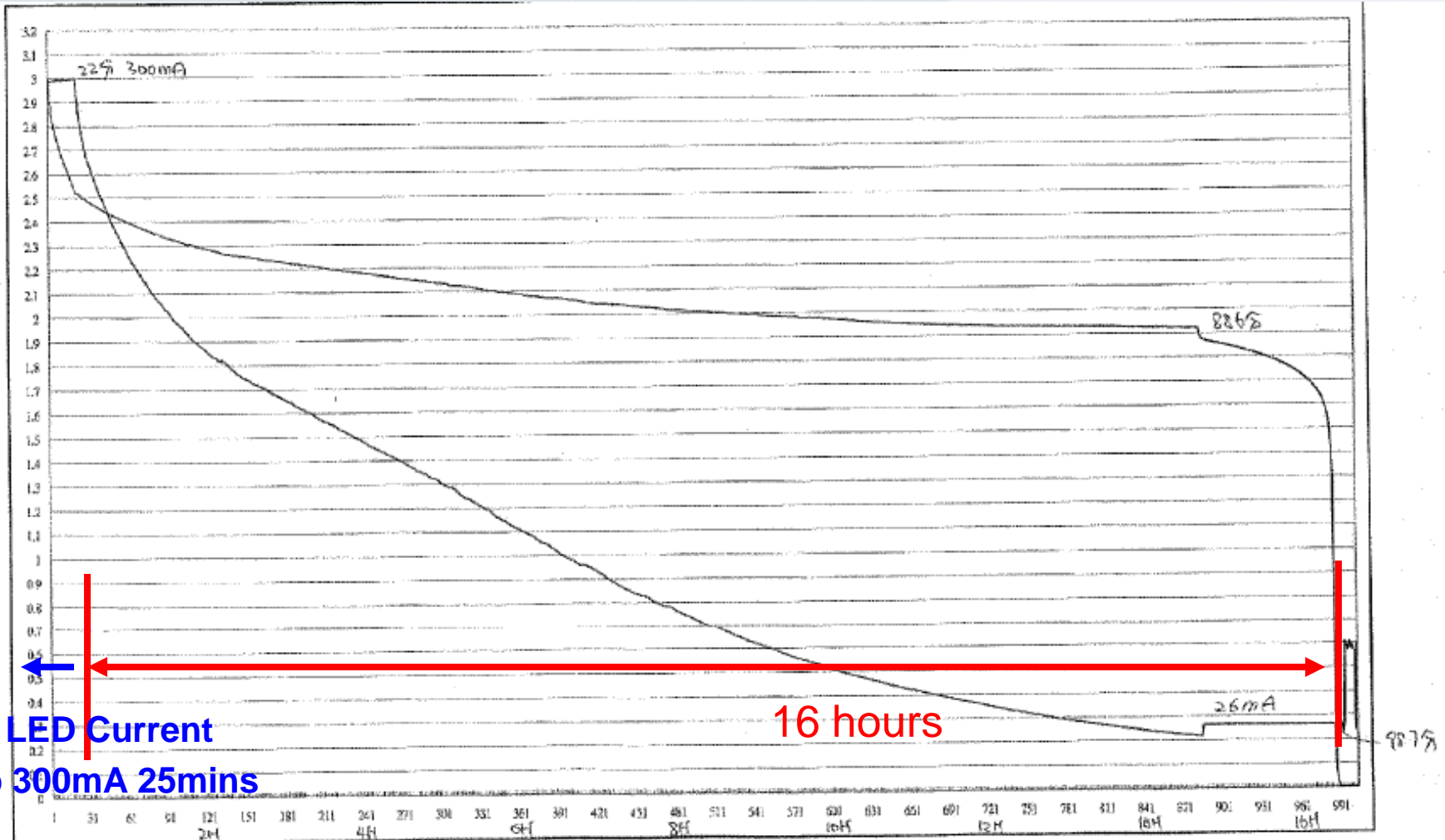


LED Current  
up 300mA 25mins

16 hours

# Luminance Comparison


illuminance v.s. time @ 4 meter

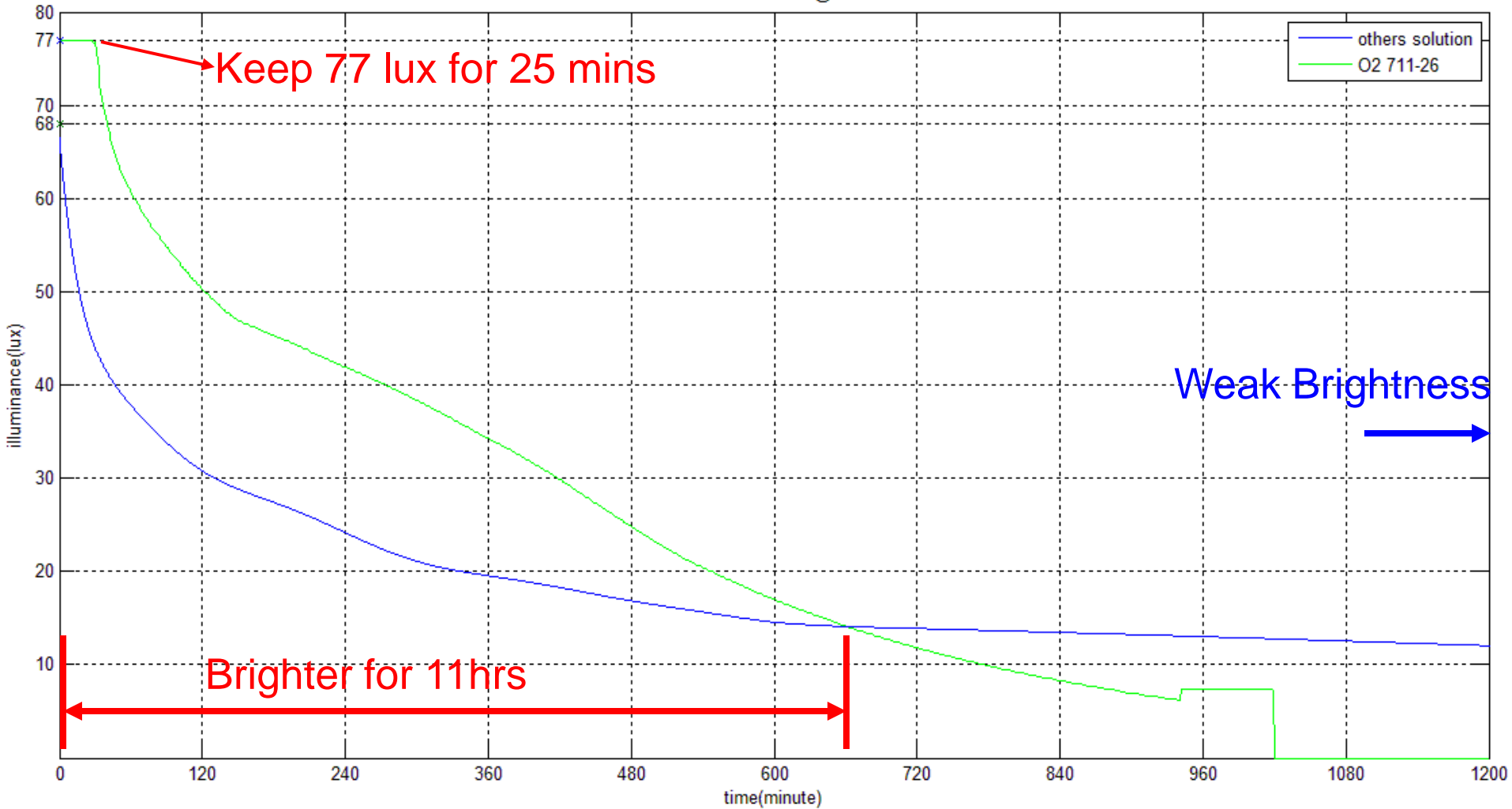


# Comparison Advantage

- **Smaller PCB, fewer component**
  - Support 1 Alkaline PCB size
- **Startup Voltage from 0.8V**
  - Build in MOSFET


Popular solution

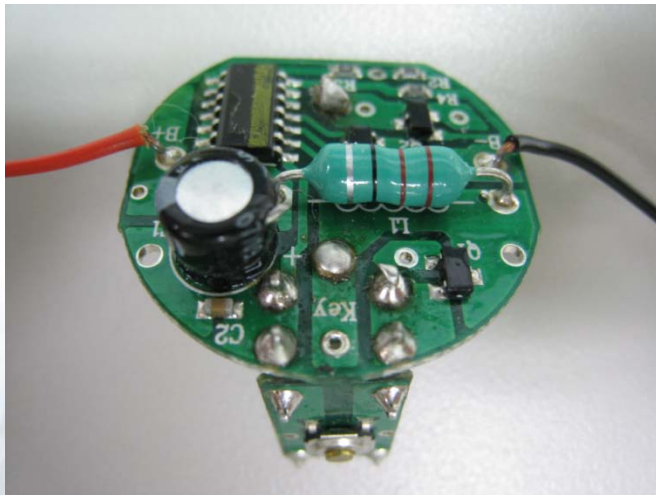

Our solution

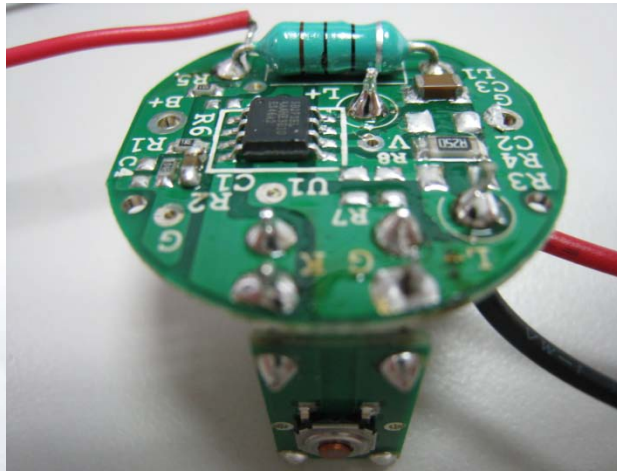

1 Alkaline

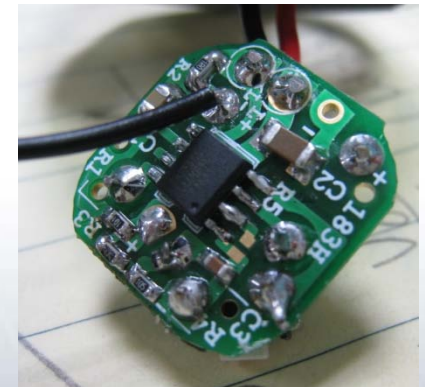





# Comparison Advantage

- **Protect LED over current at beginning**
  - MCU solution cause 440mA initial
- **Insure constant LED current in MP stage**
  - MOSFET & inductor tolerance cause LED current variation
- **Provide life time for user define**

Popular solution

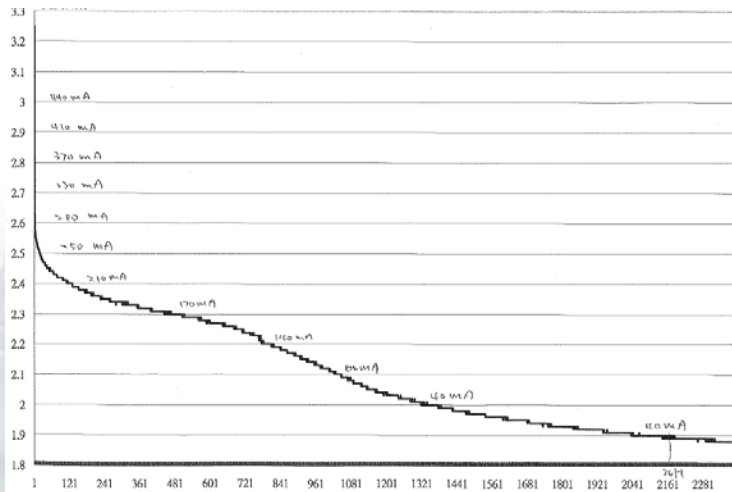

Our solution

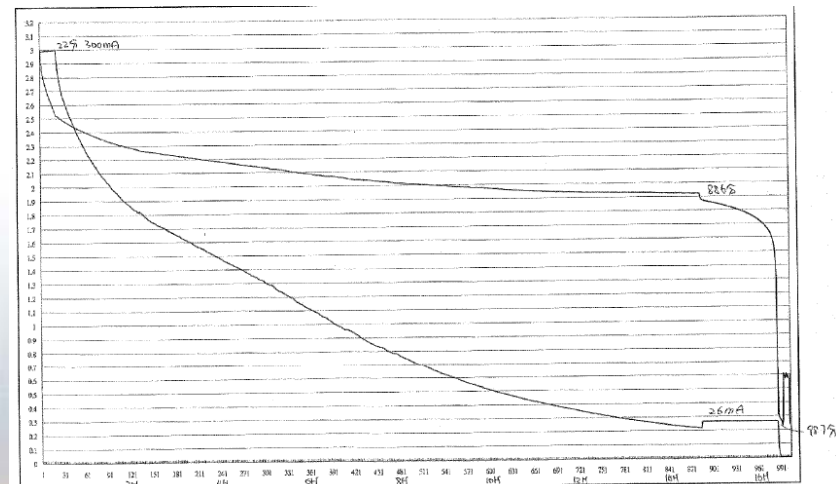





# Bikehawk\_BC

- More Charger Battery need in the future (Li or NimH)
- Develop IC for both charger and constant LED current
- Supports 1 Li-ion or 2-4 cell NimH batteries
- Automatic switching between constant current and constant voltage mode
- Over charge protection
- Automatic recharge
- Low-Battery, Battery full and charging STATUS output
- Drives up to 1-3 high brightness LEDs with forward current 350mA
- Supports both boost and/or buck mode operation

# Current Solution


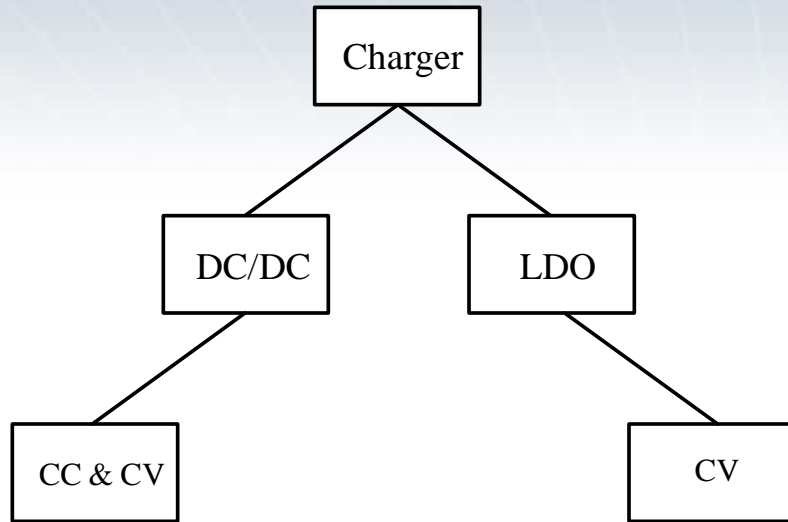


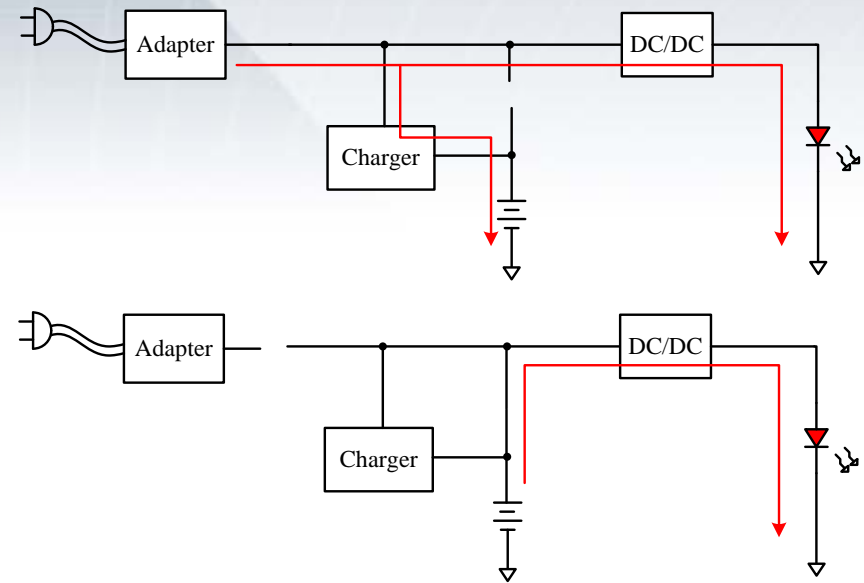- ∨ LDO Disadvantage
  - Less Efficiency
  - Non Fast Charger



- ∨ Traditional switching topology
  - Larger PCB size - 2 power chains

# Bikehawk\_BC Future

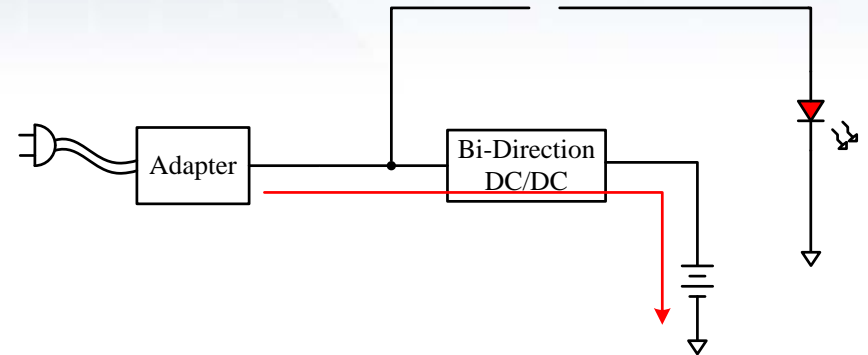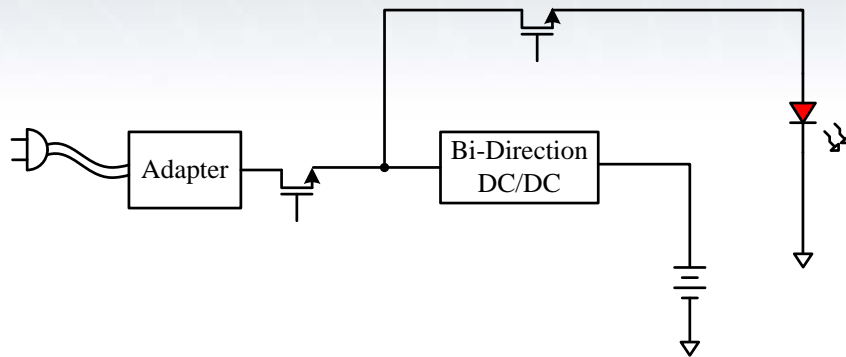


✓ New Patent Idea!


Fast Charger and constant LED current Controller integrated

✓ Reduce to one single power chain??

- Less Cost
- Saving Area

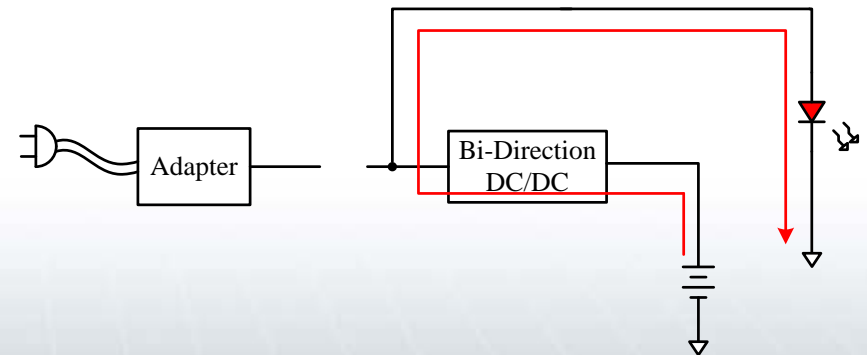

# BikeHawk\_BC Schematic

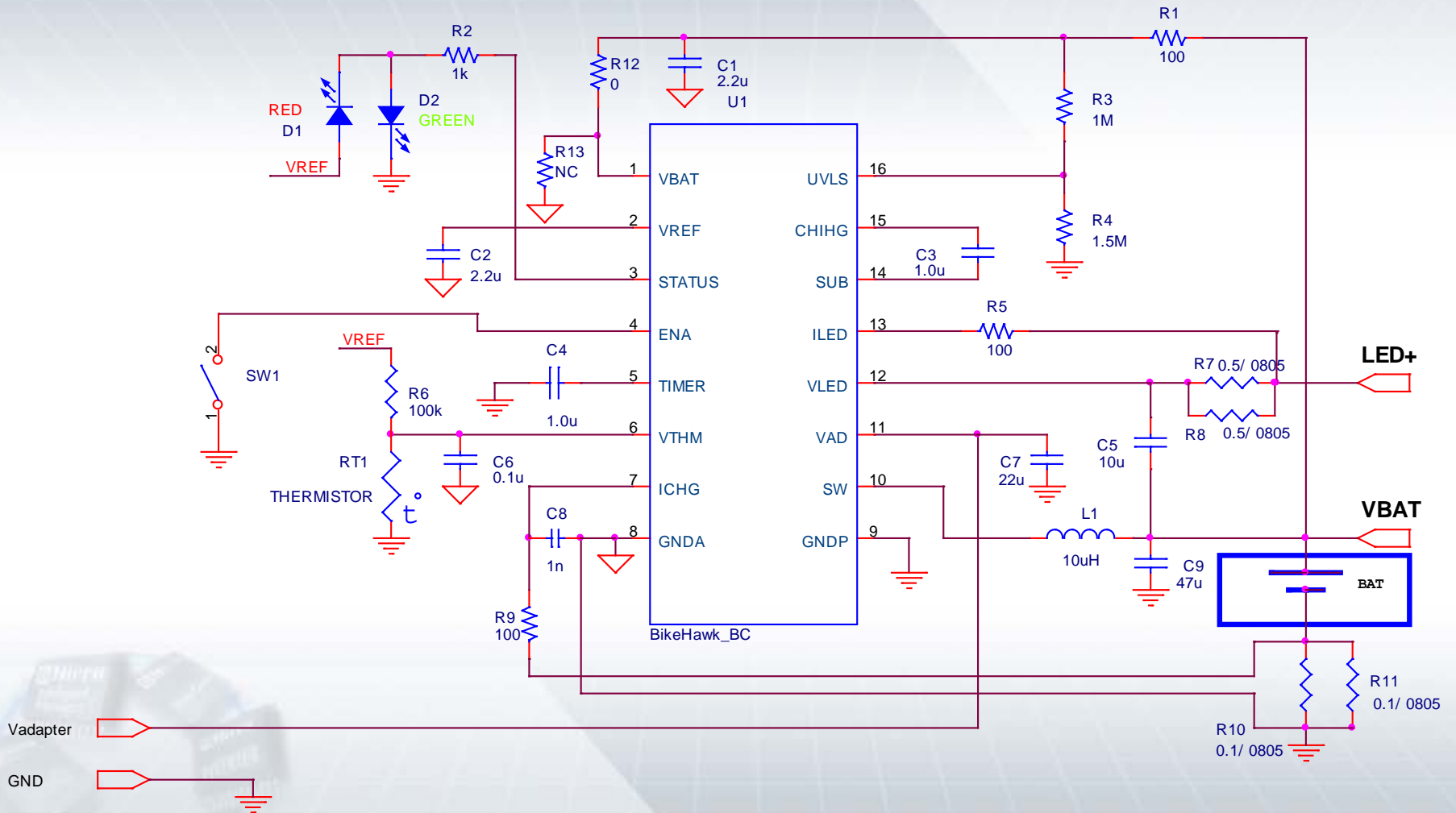

- Solution Provider
- Full Experience of Your Life
- Good Hobby
- Patent Skill

# Survival Skill in Job---

---1---

**批判思考與解決問題**  
能夠問對問題，是  
批判思考、解決問題  
的第一步

---2---

**跨界合作與  
以身作則的領導**  
你不再只是跟這棟樓的人  
工作，而是跟不同國家、  
領域、文化的人合作，  
過去威權式領導已越  
來越不管用



# Survival Skill in Job---

--- 3 ---

## 靈活與適應力

今天的工作未來可能不存在，必須終生學習，持續接收新資訊、新情勢，隨時應變，因為未來世界不跟學校考試一樣有標準答案

--- 4 ---

## 主動進取和創業家精神

不願意嘗試你就輸了，你必須採取主動、並富有創造力，不斷找尋新機會、點子、策略、不斷創新

# Survival Skill in Job---

---5---

## 口語和文字溝通能力

你要有**60秒**可以說服長官或客戶你的提案，以及他可以从這**60秒**的會面中可以帶走什麼的能力

--- 6 ---

## 評估和分析資料能力


資訊瞬息萬變，你有沒有能力透過多元管道取得，並分析、檢證這些資訊，批判思考力是基礎

--- 7 ---

## 好奇心與想像力

企業要的不只是聰明人，而是懂得問出好問題、追根究柢、對世界好奇的人，因為好奇和追根究柢解答了最重要的問題

發明是百分之一的靈感加上百分之九十九的血汗。

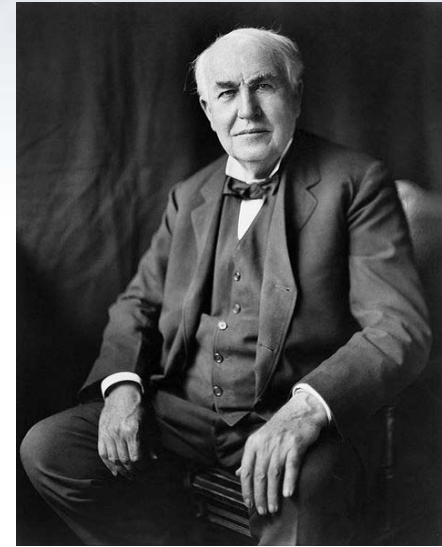

Thomas Edison

我的人生哲學是工作，我要揭示大自然的奧秘。並以此為人類造福。我們活著的短暫一生中，我不知道還有什麼比這種服務更好的了。